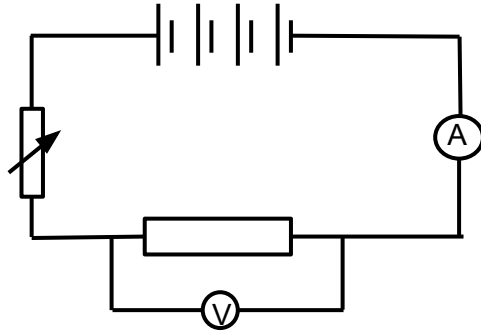


Ohms Law Graphs



In this experiment a resistor is connected to a battery.
A v _____ across the resistor measures the pd across it.
The ammeter measures the c _____ through it.
The amount of current going into the resistor can be varied using the v _____ r _____.
For each graph below find the value of the resistance of the resistor

