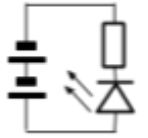



# Voltage Dividers

# Space School




In the following voltage divider circuits or, as they are otherwise called, potential divider circuits, find the missing quantity in each practice question.


(1)

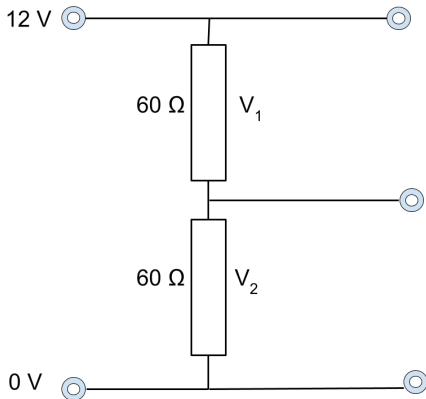


(2)

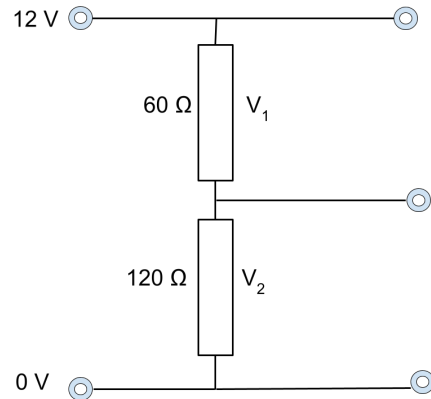


(3)

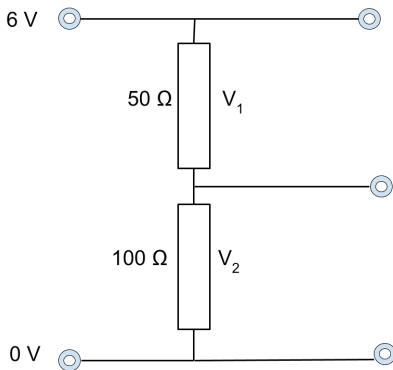


(4)

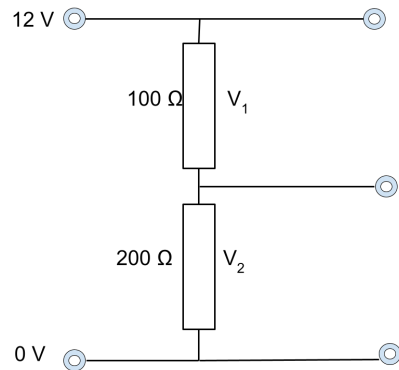


(5)

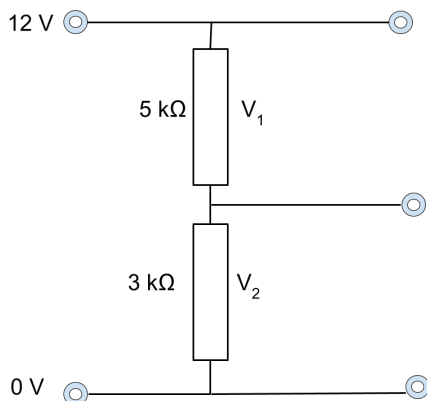


(6)

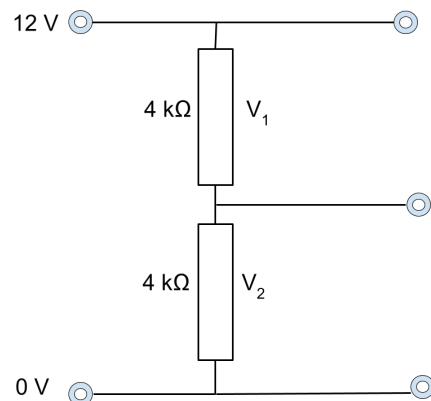


(7)

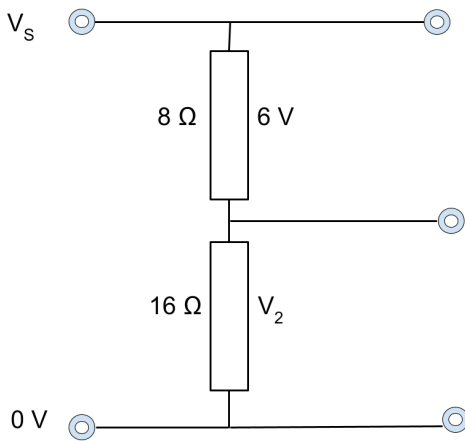


(8)

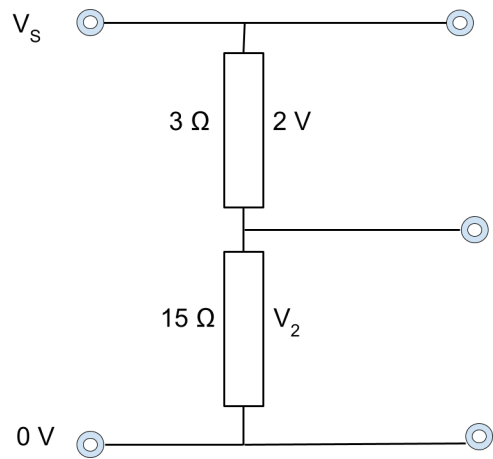

(9)

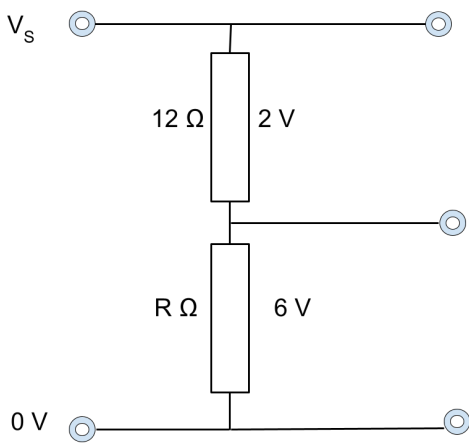


(10)

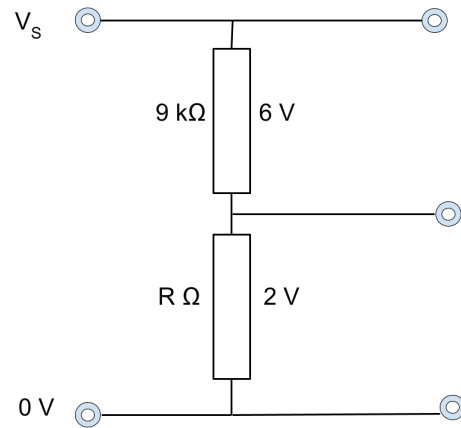

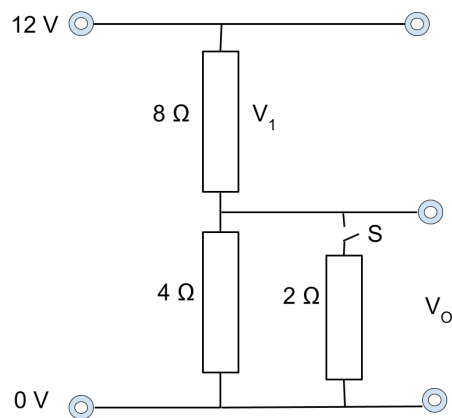(11) A potential divider circuit is shown below.

Determine the output voltage when switch S is open and then when switch S is closed.



---

**Answers:**

(1)  $V_1=6V$   $V_2 = 6V$

(2)  $V_1=4V$   $V_2 =8V$

(3)  $V_1=2V$   $V_2=4V$

(4)  $V_1=4V$   $V_2=8$

(5)  $V_1=7.5V$   $V_2=4.5V$

(6)  $V_1=6V$   $V_2= 6V$

(7)  $V_2=12$   $V_S=18V$

(8)  $V_2=10V$

(9)  $R = 36\Omega$   $V_S=8V$

(10)  $R=3\Omega$   $V_S=8V$

(11) Switch S open  $V_O=4V$ , closed  $V_O= 1.75V$

---