

Electricity




Internal Resistance

- 1) State what is meant by the **emf** of an electric cell.
- 2) A physics student measures the voltage across the terminals of an electric cell. The voltmeter connected across the terminals reads 1.5 V when no current is taken from the cell. When an electric current of 0.5 A is taken from the cell the voltmeter reads 1.3 V.

- a) State the emf of the cell. [1.5 V]
b) State the lost volts of the cell. [0.2 V]
c) Calculate the internal resistance of the cell. [0.4 Ω]

- 3) The circuit shown is built to investigate the internal resistance of an electric cell.

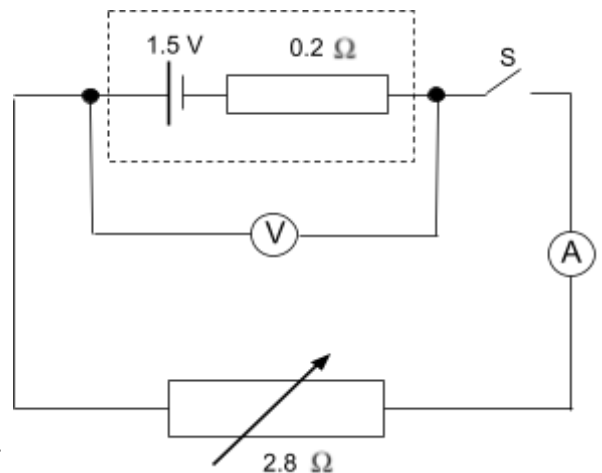
- a) State the reading on the voltmeter when the switch is open. [1.5 V]
The switch is open.
b) Determine the electric current reading on the ammeter when the switch is closed. [0.5 A]
c) Find the value of the lost volts. [0.1 V]
d) Find the terminal potential difference of the cell when the switch is closed. [1.4 V]




- 4) A physics student set up the following circuit to investigate an electric cell.

Switch S is closed and the variable resistor is changed to a resistance of 2 Ω .

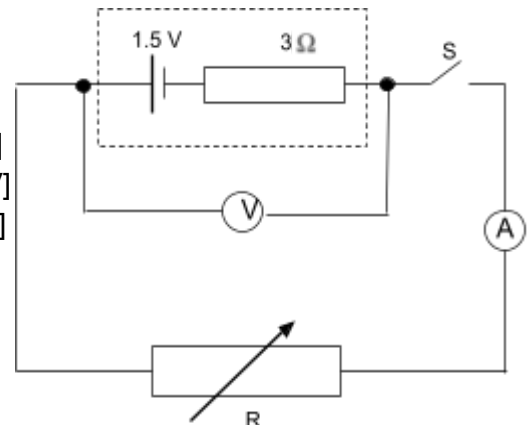- a) Calculate the reading on the ammeter. [0.3 A]
b) Find the lost volts. [0.9 V]
c) Find the tpd of the cell. [0.6 V]
d) The current is reduced in the circuit. What happens to the reading on the voltmeter? [increases]



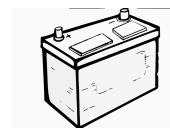
- 5) The tpd of a car battery when a voltmeter is connected across the terminals is 12.2 V
When the car battery is connected to a lamp the tpd decreases to 11.6 V and the current taken from it is 0.2 A.



- State the emf of the cell [12.2 V]
- State the lost volts [0.6 V]
- Calculate the internal resistance of the car battery. [3 Ω]

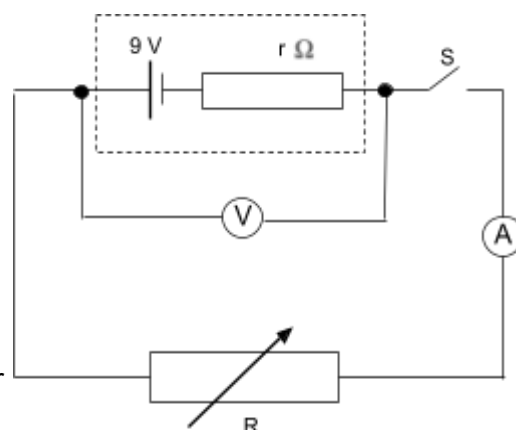- 6) When switch S is open the voltmeter across the terminals of the cell reads 9 V.
When the switch is closed the voltmeter reads 6 V and the ammeter reads 0.6 A.

- Calculate the value of the internal resistance of the cell. [5 Ω]
- Find the value of the variable resistor. [10 Ω]
- Explain what would happen to the value of the voltmeter if the resistance of the variable resistor was increased.



- 7) In the circuit shown the variable resistor is set to a value of 15 Ω . When switch S is closed, the ammeter reads 0.50 A.

- Find the tpd. [7.5 V]
- Determine the lost volts. [1.5 V]
- Calculate the internal resistance of the cell. [3 Ω]

