

# Electricity



## Internal Resistance Graphs

A physics pupil varied the current taken from some electric cells. From the graphs determine the (i) *emf of the cell*, (ii) *the internal resistance of the cell* and the (iii) *short circuit current*.



